

High Voltage Lab

DIY electronics - FREE circuit diagrams

Field-strength meter

Search

Home

Browse diagrams

Privacy policy

Contact

recent searches: remote control light on/off circuit, digital clock, li-ion charger, uninterruptable power supply, electronic pendulum, delay on Relay, amplifier for a home studio, autoVolt Regulated, motorcycle battery charger, re-model of npn transistor,

Audio

Power

Radio

Light, LED

Tools

Telephone

Automotive

MCU

Control

Timers

Misc

How to build Field-strength meter

Circuit diagram

L - 6-8 turns, 5mm dia.
C - 100p to 1n

Original source:

I saw this circuit in an old issue of "73 Radio Electronics". I built it, but it didn't work well, so I changed a few components to get better sensitivity.

Description:

This is a very straightforward circuit. The first stage acts as a crystal receiver. Use a germanium detector diode (like 1N34, but AA119 is much more common in Europe), a silicon one won't do. The frequency is determined by L and C. For the FM band and VHF, wind a coil 5mm in diameter, 6-8 turns of coated wire 1mm thick. You can always vary the frequency by spacing

the turns a bit looser or tighter. C is much less critical. Something around 100p is preferable, though. The second stage is based around the versatile 2N3819 JFET high-impedance amplifier. With the 470k potentiometer you can adjust sensitivity of the circuit. The trimmer is used to zero the meter. Use any old 50mA or slightly smaller ammeter from the junk box.

Problems:

You can't expect great performance from such a simple detector-based meter. Sensitivity is just adequate enough to get a basic idea of the power that your transmitter is capable of.

Possible uses:

Use the field-strength meter to find out when a transmitter is operating at optimal power. It can be very handy when aligning stages (like in case of the 4W transmitter) or experimenting with different antennas.

Author: 73 Radio Electronics

Email:

Website: <http://www.electronics-lab.com>

Similar diagrams

PIN NO.	E
1	Cathode E
2	Cathode D
3	Com. Anode
4	Cathode C
5	Cathode D.P.
6	Cathode B
7	Cathode A
8	Com. Anode
9	Cathode F
10	Cathode G

Led display digital Voltmeter

Digital Voltmeter

Digital Radar Speedometer



Capacitance Meter

Field-strength meter

Digital Remote Thermometer

www.high-voltage-lab.com/229/field-strength-meter

1/2

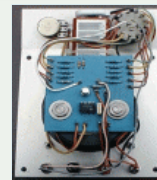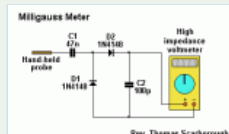**Linear Resistance Meter****MILLIGAUSS METER.****Important!!!**

We are not responsible for any injuries or damage caused by information from this website! Working with electricity is dangerous for your life, especially diagrams related to high voltage! We do not guarantee success in building devices using our diagrams! They are not tested by us. For questions about diagrams use author info below diagram or our contact page. Thank you!

[Home](#) [Browse diagrams](#) [Contact](#)

Copyright © 2022
page rendered in : 0.0621s